

1. How Hamming(7,4) works

111	110	101	100	011	010	001
7	6	5	4	3	2	1
D3	D2	D1	C2	D0	C1	C0

a. Each data bit must be covered (checked) by at least 2 parity bits

b. Why we start numbering from 1

c. Which parity bits check which data bits

i. C0

ii. C1

iii. C2

iv. If we had a C3

v. In general

d. Why we can XOR to determine the bit position

e. Expanding it further

i. Expanding to cover a larger data size

ii. Covering more errors

1. Given T errors

2. Sequential circuits
 - a. So far, only discussed combinational circuits


b. Sequential circuits

c. Examples

3. Latches

a. S-R latches

b. S-R latch implementation

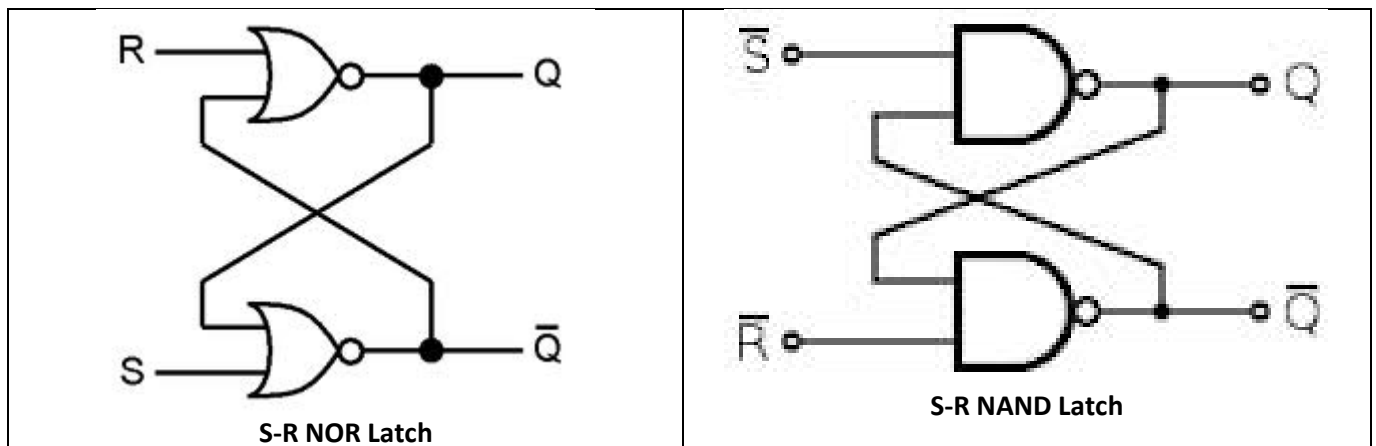

c. Characteristic tables

S	R	Q_{n+1}
0	0	
0	1	
1	0	
1	1	

S-R NOR Latch


S	R	Q_{n+1}
1	1	
1	0	
0	1	
0	0	

S-R NAND Latch


- d. State transition table for S-R NOR latch

State Transition Table for S-R NOR Latch				
Present Inputs		Present State	Next State	Type of Circuit
S	R	Q	Q'	
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

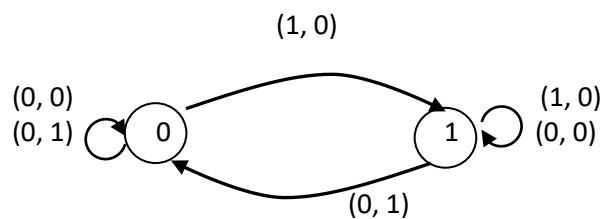
- e. State transition diagram
- Visual representation of circuit's output based on current state and input
 - For every state, all possible output combinations need to be listed



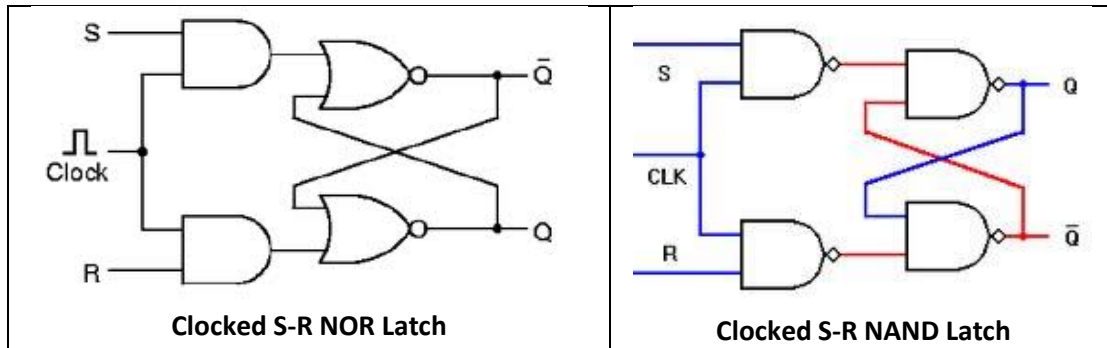4. Other latches
 - a. Clocking the latches



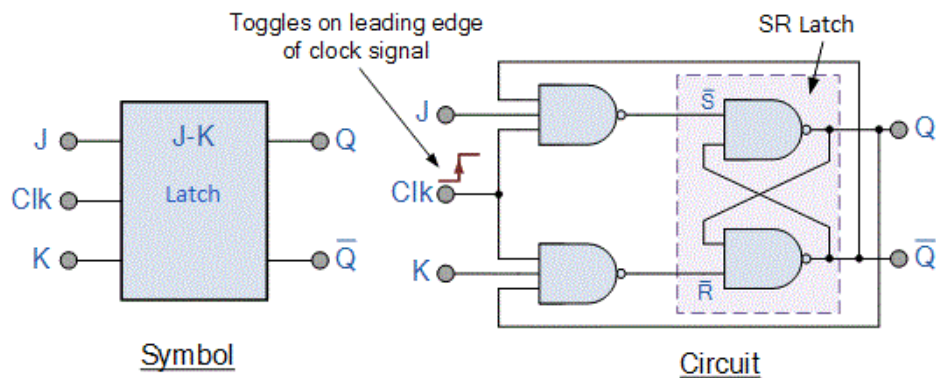- b. Clocked J-K latch
 - i. Like a S-R latch



- b. Clocked D latch

