
 


1. More on Karnaugh maps
 - a. Further example with don't cares and wrapping
 - i. $f_3 = m_0 + D_2 + D_5 + D_7 + m_8 + m_{10} = \overline{B}D$

		AB			
		00	01	11	10
CD	00	1	0	0	1
	01	0	d	0	0
	11	0	d	0	0
	10	d	0	0	1

- ii. Whether or not don't cares are included depends on your desired use case
 - i. Example: whenever we see an illegal input, raise a flag
 - ii. Wouldn't want to include don't cares in this case

 
2. Timing
 - a. Worst case path
 - i. Route through a circuit that takes the longest
 1. "Longest" can be number of gates or time, see below
 - ii. In the example on next page, worst case path is 3 gates
 1. Either A -> NOT -> AND -> OR or B -> NOT -> AND -> OR
 2. See below for time
 - iii. Worst case path determines clock speed
 1. Need to wait for all gates to finish to get output before we start new clock cycle
 - iv. Can also assign times to each type of gate to determine time output is generated
 - b. Timing diagram
 - i. Visual representation of truth tables at different parts of a digital logic circuit
 - ii. Initial values of inputs iterate over all possible combinations (like a truth table)
 - iii. Truth values at later points are shown based on each of those combinations
 - c. Example
 - i. Implementation of XOR using only AND, OR, NOT on next page
 1. $A \oplus B = A * \sim B + \sim A * B$
 - ii. Assume that we have the following gate delays
 1. NOT = 3 ns
 2. AND = 5 ns
 3. OR = 4 ns
 - iii. What is the clock time of the circuit, if inputs become valid at time 0 ns?
 1. A -> NOT -> AND -> OR (other worst case path has identical times)
 2. 0 ns + 3 ns + 5 ns + 4 ns = 12 ns



3. Combinational circuit building blocks
 - a. Talked about gates so far
 - b. We now move on to other important pieces of digital design
 - c. These pieces build upon the gates that we just learned

4. Multiplexors

 - a. Also known as MUXes
- b. MUXes select one output from multiple inputs
 - i. Used to control signal and data routing
- c. For n data inputs, a MUX has $s = \lceil \log_2 n \rceil$ select bits that control which input we select
- d. Implementation
 - i. n AND gates
 1. Each one has one data input
 2. Also has s select inputs
 3. The select inputs are all true for only one AND gate at a time
 - ii. One OR gate
 1. n inputs from the AND gates
 2. Only one of the AND gates will have a non-zero output (unless that gate's output is all zeroes)
- e. Example
 - i. 2 to 1 MUX



ii. 4 to 1 MUX

