 


1. Minimization



Original state diagram

Minimized state diagram

2. Some definitions
 - a. *Equivalent*


- b. *Successor*

- c. *Block*

- d. *Partition*


3. Partition minimization procedure

 - a. Will use the unminimized edge detector FSM for the rest of this example



- b. P_1

c. P_2

 


d. P_3

e. Further partitions

f. Look at P_4 now

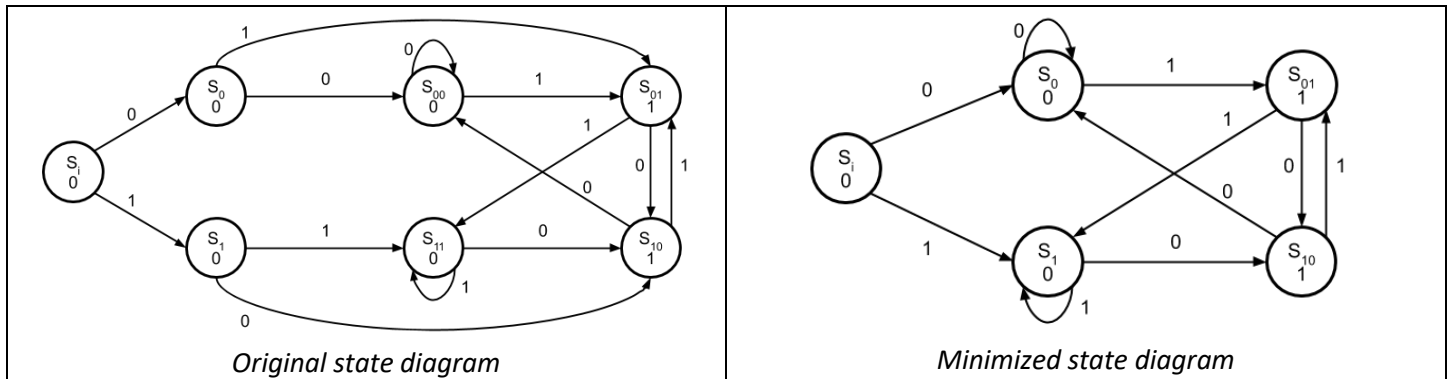g. Now use this to create minimized state diagram



4. Implementing the minimized FSM

Present State	Next State		Output z
	$x = 0$	$x = 1$	
i	0	1	0
0	00	01	0
1	10	11	0
00	00	01	0
01	10	01	1
10	00	01	1
11	10	11	0

Original state table

Present State	Next State		Output z
	$x = 0$	$x = 1$	
i			
0			
1			
01			
10			

Minimized state table

- a. Next, assign binary codes in state transition table

Present State	Next State		Output z
	$x = 0$	$x = 1$	
i	0	1	0
0	0	01	0
1	10	1	0
01	10	1	1
10	0	01	1

Present State	Binary Code	Present State			Input x	Next State			Output z
		A	B	C		A'	B'	C'	
i	000								
i	000								
0	001								
0	001								
1	010								
1	010								
01	011								
01	011								
10	100								
10	100								

Present State	Binary Code	Present State			Input x	Next State			Output z
		A	B	C		A'	B'	C'	
i	000	0	0	0	0	0	0	1	0
i	000	0	0	0	1	0	1	0	0
0	001	0	0	1	0	0	0	1	0
0	001	0	0	1	1	0	1	1	0
1	010	0	1	0	0	1	0	0	0
1	010	0	1	0	1	0	1	0	0
01	011	0	1	1	0	1	0	0	1
01	011	0	1	1	1	0	1	0	1
10	100	1	0	0	0	0	0	1	1
10	100	1	0	0	1	0	1	1	1

- Create K-maps for each flip flop based on input and present state
- Create a K-Map based on flip-flops to determine the output combinational circuit

A'

		AB			
		00	01	11	10
Cx	00				
	01				
	11				
	10				

B'

		AB			
		00	01	11	10
Cx	00				
	01				
	11				
	10				

C'

		AB			
		00	01	11	10
Cx	00				
	01				
	11				
	10				

z

		AB			
		00	01	11	10
C	0				
	1				