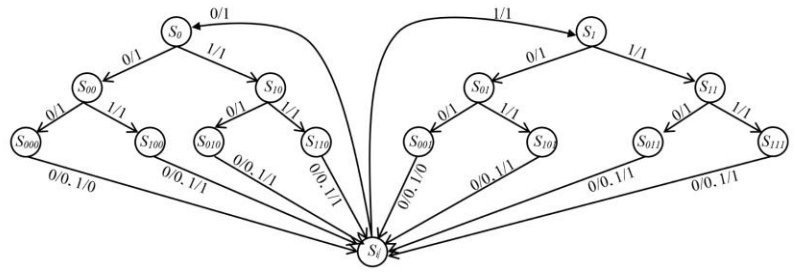


1. Mealy model example
 - a. Design a circuit
 - b. State transition diagram

2. Minimizing a Mealy model



a. P_1

b. P_2

c. P_3

d. P_4

e. P_5

3. Implementing the FSM

State transition diagram

Present State	Next State		Output	
	x = 0	x = 1	x = 0	x = 1
<i>i</i>				
*				
0*				
1*				
00*				
~(00*)				

State table

4. Optimal assignment of binary codes

a. Rule of thumb for state binary code assignments

b. Assign using the rules above

Present State	Next State		Output	
	x = 0	x = 1	x = 0	x = 1
<i>i</i>	*	*	1	1
*	0*	1*	1	1
0*	00*	~(00*)	1	1
1*	~(00*)	~(00*)	1	1
00*	<i>i</i>	<i>i</i>	0	0
~(00*)	<i>i</i>	<i>i</i>	0	1

		<i>AB</i>			
		00	01	11	10
<i>C</i>	0				
	1				

c. Note that there may potentially be more than one valid code assignment that minimizes distance

- d. Make state transition table from the above with assigned binary codes

Present State	Next State		Output	
	x = 0	x = 1	x = 0	x = 1
<i>i</i>	*	*	1	1
*	0*	1*	1	1
0*	00*	~(00*)	1	1
1*	~(00*)	~(00*)	1	1
00*	<i>i</i>	<i>i</i>	0	0
~(00*)	<i>i</i>	<i>i</i>	0	1

		<i>AB</i>			
		00	01	11	10
<i>C</i>	0	<i>i</i>	*	0*	00*
	1	~(00*)	1*		

Present State	Binary Code	Present State			Input <i>x</i>	Next State			Output <i>z</i>
		<i>A</i>	<i>B</i>	<i>C</i>		<i>A'</i>	<i>B'</i>	<i>C'</i>	
	000	0	0	0					
	000	0	0	0					
	001	0	0	1					
	001	0	0	1					
	010	0	1	0					
	010	0	1	0					
	011	0	1	1					
	011	0	1	1					
	100	1	0	0					
	100	1	0	0					
	101	1	0	1					
	101	1	0	1					
	110	1	1	0					
	110	1	1	0					
	111	1	1	1					
	111	1	1	1					

- Create K-maps for each flip flop based on input and present state in table above
- Create a K-Map based on flip-flops to determine the output combinational circuit

Present State	Binary Code	Present State			Input x	Next State			Output z
		A	B	C		A'	B'	C'	
i	000	0	0	0	0	0	1	0	1
i	000	0	0	0	1	0	1	0	1
$\sim(00^*)$	001	0	0	1	0	0	0	0	0
$\sim(00^*)$	001	0	0	1	1	0	0	0	1
$*$	010	0	1	0	0	1	1	0	1
$*$	010	0	1	0	1	0	1	1	1
1^*	011	0	1	1	0	0	0	1	1
1^*	011	0	1	1	1	0	0	1	1
00^*	100	1	0	0	0	0	0	0	0
00^*	100	1	0	0	1	0	0	0	0
	101	1	0	1	0	d	d	d	d
	101	1	0	1	1	d	d	d	d
0^*	110	1	1	0	0	1	0	0	1
0^*	110	1	1	0	1	0	0	1	1
	111	1	1	1	0	d	d	d	d
	111	1	1	1	1	d	d	d	d

A'

		AB			
		00	01	11	10
Cx	00				
	01				
	11				
	10				

B'

		AB			
		00	01	11	10
Cx	00				
	01				
	11				
	10				

C'

		AB			
		00	01	11	10
Cx	00				
	01				
	11				
	10				

z

		AB			
		00	01	11	10
Cx	00				
	01				
	11				
	10				

- Use derivations from the K-maps to design initial combinational circuit